

a) $A = 10 \text{ V}$


$$\frac{B}{1000} + \frac{B-A}{2000} + \frac{B}{2000} + \frac{B-C}{3000} = 0 \Rightarrow 6B + 3B - 3A + 3B + 2B - 2C = 0 \\ 14B - 2C = 30$$

$$\frac{C}{1000} + \frac{C-B}{2000} = 0 \Rightarrow 3C + C - B = 0 \\ 4C = B$$

$$\Rightarrow 14(4C) - 2C = 30 \quad C = \frac{30}{54} \text{ V}, \quad B = 4C$$


$$V_x = B = \frac{120}{54} \text{ V}$$

b) Simplify

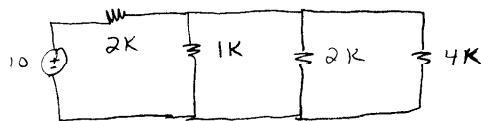


$$\frac{1}{R_{\text{EQ}}} = \frac{1}{4k} + \frac{1}{2k} + \frac{1}{1k} \\ = \frac{1+2+4}{4k} \Rightarrow$$
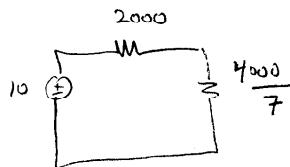
$$R_{\text{EQ}} = \frac{4000}{7} \Omega$$



$$V_x = 10 \left(\frac{\frac{4000}{7}}{\frac{2000}{7} + \frac{4000}{7}} \right) = \frac{120}{54} \text{ V}$$

(2)

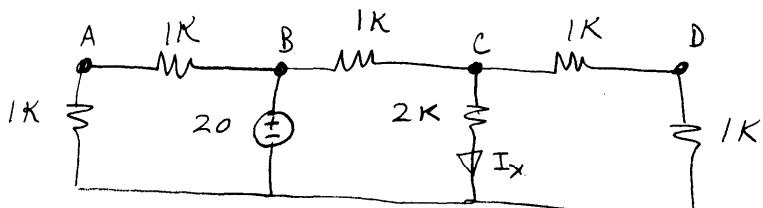

a) $\frac{A-B}{1000} + \frac{A}{1000} = 0 \Rightarrow A = \underline{B/2}$

B = 20

$$\frac{C-D}{1000} + \frac{C}{2000} + \frac{C-D}{1000} = 0 \Rightarrow \underline{2C - 2D + C + 2C - 20 = 0}$$



$$\underline{5C - 2D = 40}$$

$$\frac{D-C}{1000} + \frac{D}{1000} = 0 \Rightarrow \underline{D = C/2}$$

$\Rightarrow 5C - C = 40 \quad \underline{C = 10 \text{ V}}$

$$I_x = \frac{10 \text{ V}}{2000} = \underline{5 \text{ mA}}$$

b)

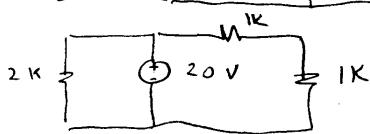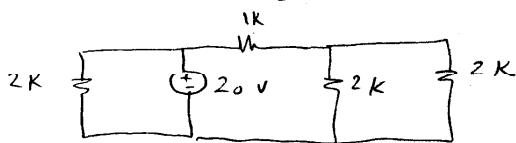

$$V_{1K} = 20 \left(\frac{1000}{1000+1000} \right) = 10 \text{ V}$$

\therefore there are 10V across 2K resistor, and

$$I_x = \frac{10 \text{ V}}{2000} = \underline{5 \text{ mA}}$$